 


The Solution of First Term Examination (4th Class)
2010-2011

Q1) Use *T-flip-flops* to design a *Mealy* system that produces a 1 output if there have been *four or more* consecutive 1 inputs or *two or more* consecutive 0 inputs.

Solution:

We start with a state for which the last input is (0). From there, we need four consecutive (1's) to get a (1) output or another (0). Thus, on additional (0's), we loop back to state (A). On a (1), we go to (B); on a second (1), we go to (C); and on a third (1), we go to (D). In (D), additional (1's) produce a (1) output; (0's) return the system to state (A). The state diagram will be as follows:




The state table will be as follows:

Present State	Next State		Output	
	X=0	X=1	X=0	X=1
A	A	B	1	0
B	A	C	0	0
C	A	D	0	0
D	A	D	0	1

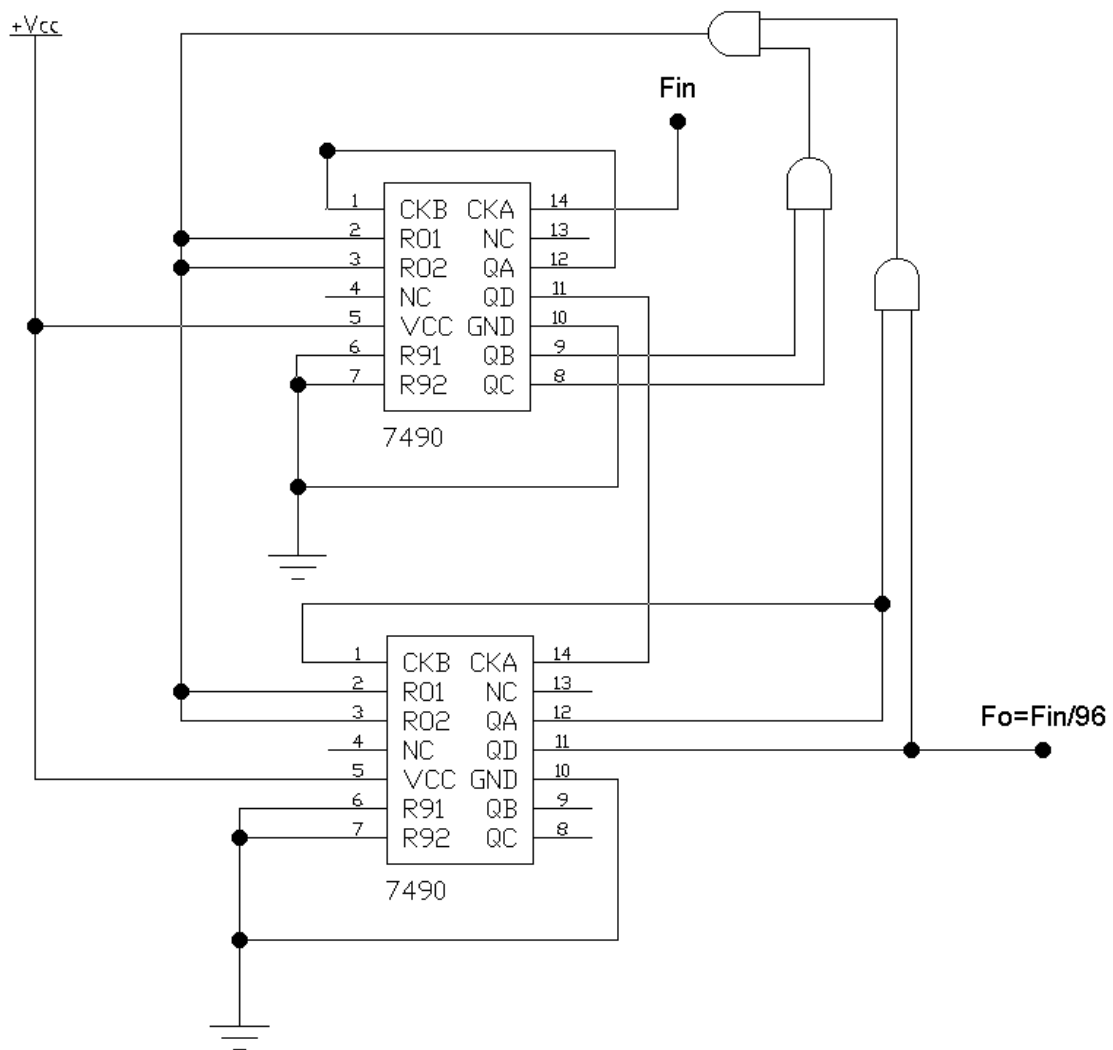Q2) Design a **MOD-96** asynchronous counter using minimum number of **74LS90s** ICs.
Explain how the **MOD-96** circuit functions, based on the count sequence and decoding operations.

Solution:

The designed circuit of MOD-96 by using two ICs of **74LS90s** asynchronous counter as shown in figure below:



Q3) Table (1) gives the excitation table of a certain flip-flop having (X_1 & X_2) as its inputs. Draw the circuit excitation table of an **MOD-5** synchronous counter using this flip-flop for the count sequence (**0, 1, 3, 5, 6, 0, ...**). If the present state is an undesired one, it should transit to (**6**) on application of a clock pulse. Design the counter circuit using the flip-flop whose excitation circuit is given in Table (1).

Table (1)

Present state (Q_n)	Next state (Q_{n+1})	Inputs	
		X_1	X_2
0	0	0	0
0	1	0	1
1	0	1	X
1	1	X	1

Solution:

- The circuit excitation table is shown in Table (2).
- The number of flip-flops required is (3).
- $X_1(A)$ and $X_2(A)$ are the inputs of flip-flop (A), which is also the LSB flip-flop.
- $X_1(B)$ and $X_2(B)$ represent the inputs to flip-flop (B).
- $X_1(C)$ and $X_2(C)$ are the inputs to flip-flop (C), which is also the MSB flip-flop.
- The next step is to draw Karnaugh maps, one each for different inputs to the three flip-flops.
- Figures (1)(a) to (f) show the Karnaugh maps for $X_1(A)$, $X_2(A)$, $X_1(B)$, $X_2(B)$, $X_1(C)$ and $X_2(C)$ respectively.
- The minimized expressions are as follows:
 - $X_1(A) = A.$ $X_2(A) = A + B'C'.$
 - $X_1(B) = B.$ $X_2(B) = A + B + C.$
 - $X_1(C) = C.$ $X_2(C) = B + C.$
- Figure (2) shows the circuit implementation.

Table (2)

Present state			Next state			Inputs					
C	B	A	C	B	A	$X_1(A)$	$X_2(A)$	$X_1(B)$	$X_2(B)$	$X_1(C)$	$X_2(C)$
0	0	0	0	0	1	0	1	0	0	0	0
0	0	1	0	1	1	X	1	0	1	0	0
0	1	0	1	1	0	0	0	X	1	0	1
0	1	1	1	0	1	X	1	1	X	0	1
1	0	0	1	1	0	0	0	0	1	X	1
1	0	1	1	1	0	1	X	0	1	X	1
1	1	0	0	0	0	0	0	1	X	1	X
1	1	1	1	1	0	1	X	X	1	X	1

X = don't care condition.

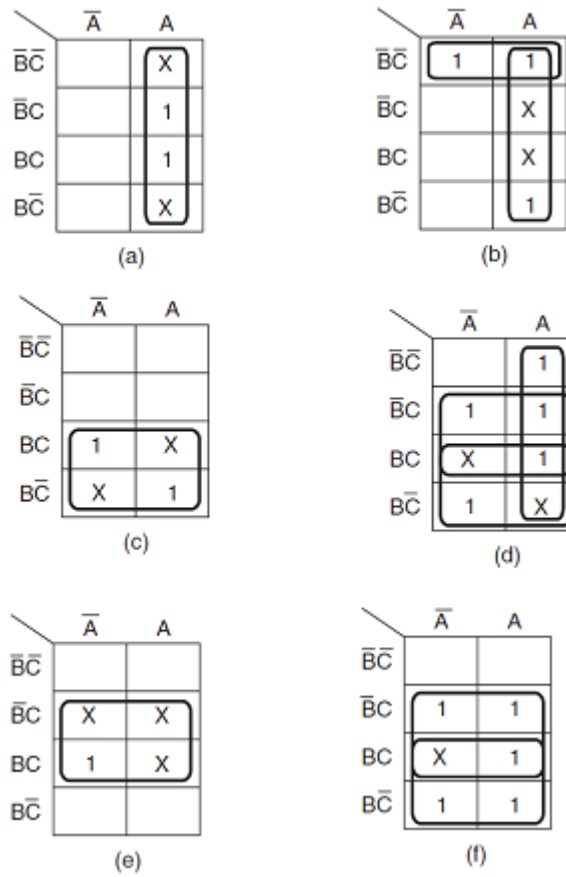


Figure (1): Karnaugh maps.

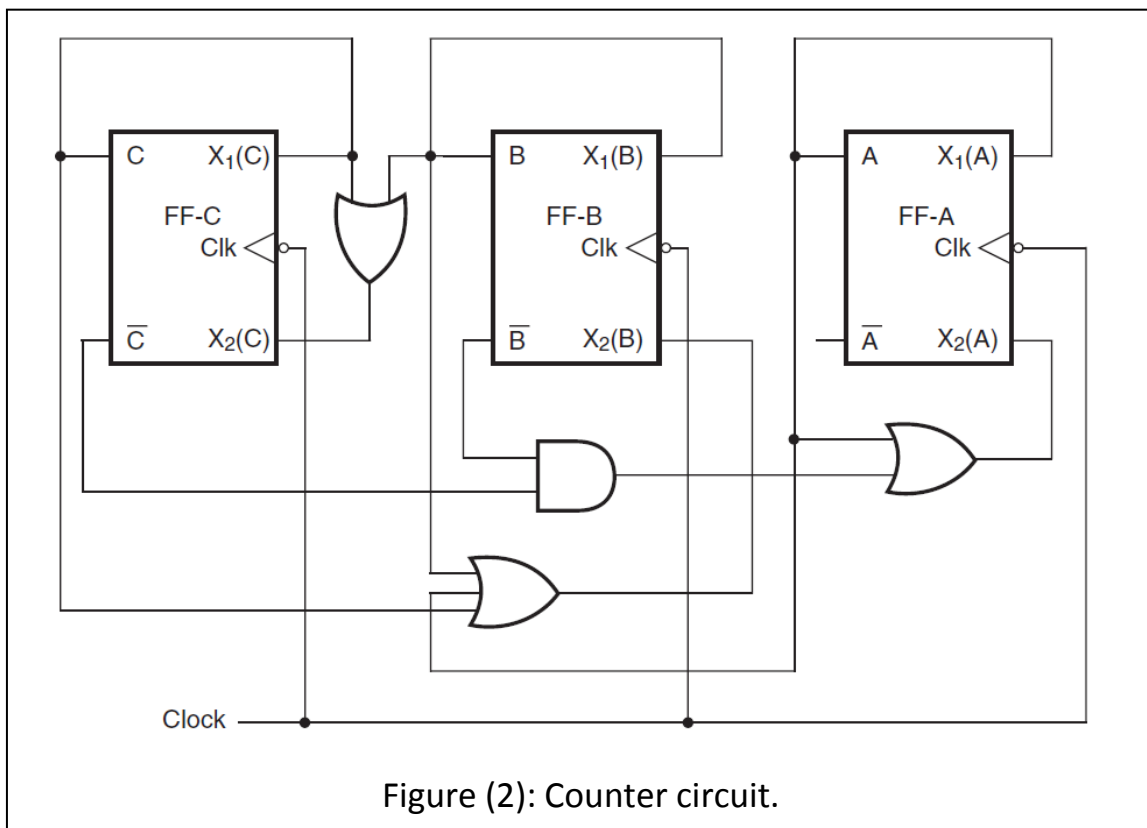


Figure (2): Counter circuit.