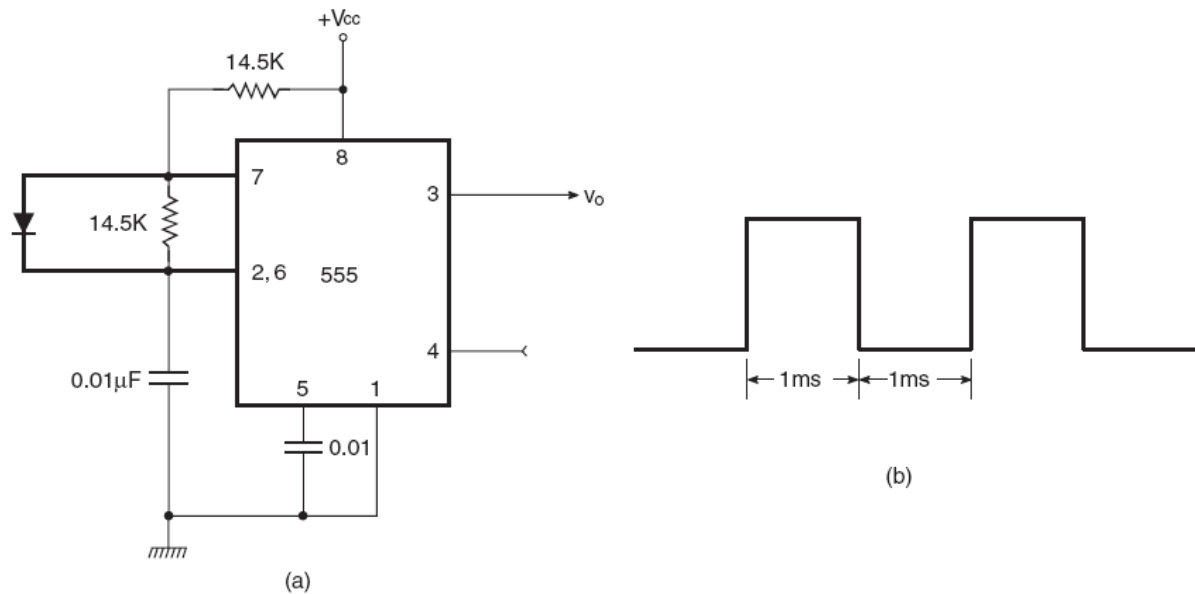


The Solution of the First Term Examination
(2008-2009)

Q1): The pulsed waveform of Fig. (b) is applied to the **RESET** terminal of the astable multivibrator circuit of Fig. (a). *Draw the output waveform.*




Solution:

The circuit shown in Fig. (a) is an astable multivibrator with a 500 Hz symmetrical waveform applied to its **RESET** terminal. The **RESET** terminal is alternately **HIGH** and **LOW** for 1.0 ms. When the **RESET** input is **LOW**, the output is forced to the **LOW** state. When the **RESET** input is **HIGH**, an astable waveform appears at the output. The **HIGH** and **LOW** time periods of the astable multivibrator are determined as follows:

$$\text{HIGH time} = 0.69 \times 14.5 \times 10^3 \times 0.01 \times 10^{-6} = 0.1 \text{ms.}$$

$$\text{LOW time} = 0.69 \times 14.5 \times 10^3 \times 0.01 \times 10^{-6} = 0.1 \text{ms.}$$

 The astable output is thus a 5 kHz symmetrical waveform. Every time the **RESET** terminal goes to **HIGH** for 1.0 ms, five cycles of 5 kHz waveform appear at the output. Figure below shows the output waveform appearing at terminal 3 of the timer IC.



Q2): Design a **3-bit up/down** synchronous counter using **T flip-flops**. It should include a control input called Up/\overline{Down} . If $Up/\overline{Down} = 0$, then the circuit should behave as a *down-counter*. If $Up/\overline{Down} = 1$, then the circuit should behave as an *up-counter*.

Solution:

The *present state – present input – next state* table will be as follows:

No.	Present State			U/D	Next State			Present Input		
	Q _C	Q _B	Q _A	C	Q _C	Q _B	Q _A	T _C	T _B	T _A
0	0	0	0	0=D	1	1	1	1	1	1
1	0	0	0	1=U	0	0	1	0	0	1
2	0	0	1	0	0	0	0	0	0	1
3	0	0	1	1	0	1	0	0	1	1
4	0	1	0	0	0	0	1	0	1	1
5	0	1	0	1	0	1	1	0	0	1
6	0	1	1	0	0	1	0	0	0	1
7	0	1	1	1	1	0	0	1	1	1
8	1	0	0	0	0	1	1	1	1	1
9	1	0	0	1	1	0	1	0	0	1
10	1	0	1	0	1	0	0	0	0	1
11	1	0	1	1	1	1	0	0	1	1
12	1	1	0	0	1	0	1	0	1	1
13	1	1	0	1	1	1	1	0	0	1
14	1	1	1	0	1	1	0	0	0	1
15	1	1	1	1	0	0	0	1	1	1

The K-map will be as follows:

		T_C			
$Q_A C$	$Q_C Q_B$	00	01	11	10
00	1				
01				1	
11				1	
10	1				

		T_B			
$Q_A C$	$Q_C Q_B$	00	01	11	10
00	1			1	
01	1			1	
11	1			1	
10	1			1	


		T_A			
$Q_A C$	$Q_C Q_B$	00	01	11	10
00	1	1	1	1	1
01	1	1	1	1	1
11	1	1	1	1	1
10	1	1	1	1	1

$$T_C = Q'_B \cdot Q'_A \cdot C' + Q_B \cdot Q_A \cdot C$$


$$T_B = Q'_A \cdot C' + Q_A \cdot C$$

$$T_A = 1$$

 The circuit diagram of the counter will be as shown below:



 Q3): Analyze the counter shown in figure below.



Solution:


From figure above we have:

$$\begin{aligned}
 J_A &= B \cdot C' & K_A &= 1. \\
 J_B &= A \cdot C + A' \cdot C' & K_B &= 1. \\
 J_C &= A' \cdot B & K_C &= A' + B.
 \end{aligned}$$

The present state – present input – next state table will be as follows:

No.	Present State			Present Input						Next State			State
	C	B	A	J _C	K _C	J _B	K _B	J _A	K _A	C	B	A	
0	0	0	0	0	1	1	1	0	1	0	1	0	2
2	0	1	0	1	1	1	1	1	1	1	0	1	5
5	1	0	1	0	0	1	1	0	1	1	1	0	6
6	1	1	0	1	1	0	1	0	1	0	0	0	0
1	0	0	1	0	0	0	1	0	1	0	0	0	0
3	0	1	1	0	1	0	1	1	1	0	0	0	0
4	1	0	0	0	1	0	1	0	1	0	0	0	0
7	1	1	1	0	1	1	1	0	1	0	0	0	0

 The state transition diagram will be as follows:



Then the counter classification is summarized here:

- MOD 4 (0, 2, 5, 6).
- Divided by 4.
- Synchronous.
- Three-bit.
- Negative edge-triggered.
- Binary up counter.
- Self-starting counter.