

## TIMER CIRCUITS

### The 555 Timer

The 555 timer is a versatile and widely used device because it can be configured in two different modes either as a *monostable multivibrator (one-shot)* or as an *astable multivibrator (oscillator)*. An astable multivibrator has no stable states and therefore changes back and forth (oscillates) between two unstable states without any external triggering.

### Basic Operation

A functional diagram showing the internal components of a 555 timer is given in Fig. (1).

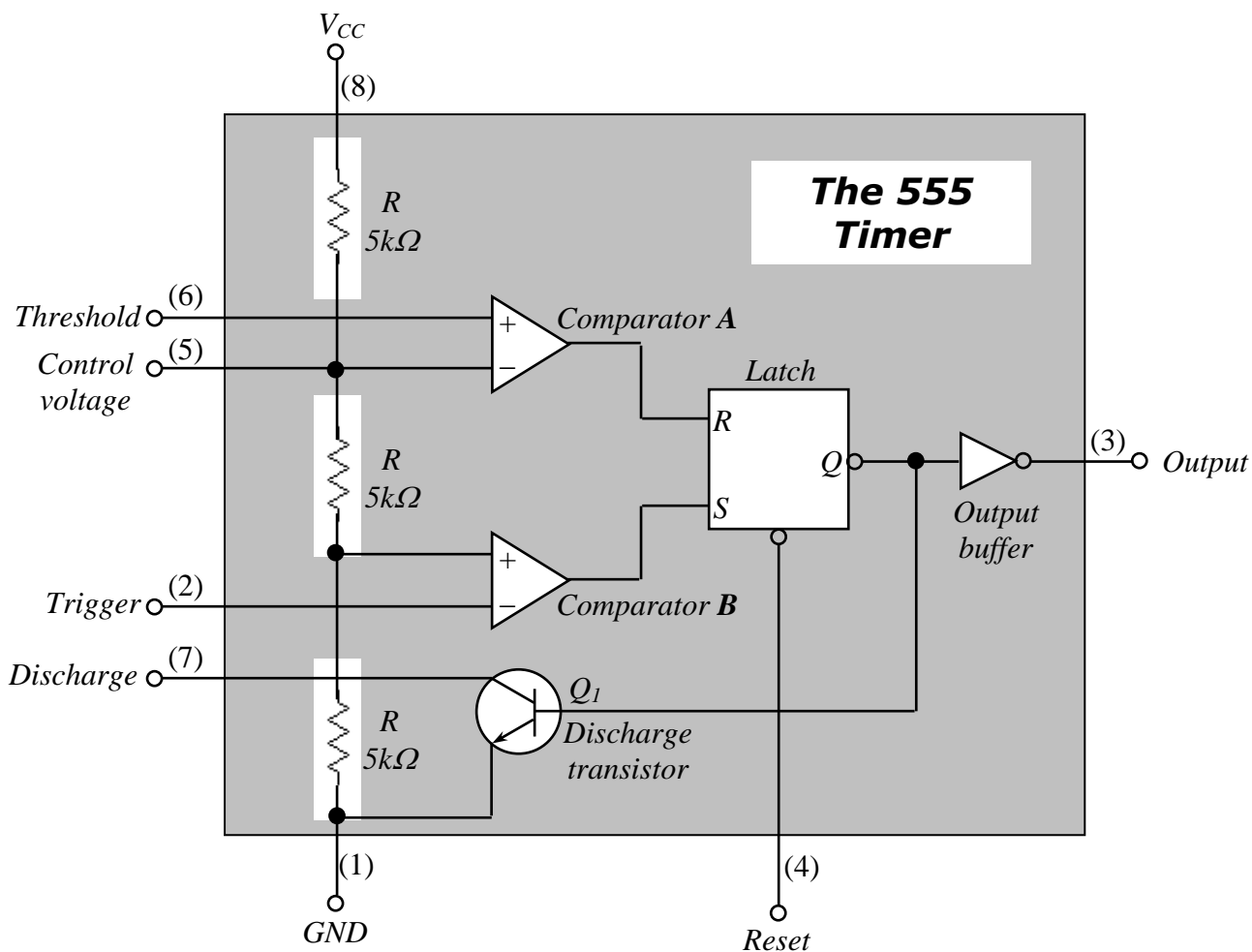


Fig. (1): Internal functional diagram of a 555 timer  
(Pin numbers are in parentheses).

The comparators are device whose outputs are **HIGH** when the voltage on the positive (+) input is greater than the voltage on the negative (-) input and **LOW** when the (-) input voltage is greater than the (+) input voltage. The voltage divider consisting of three (5-k $\Omega$ ) resistors provides a trigger level of  $1/3V_{CC}$  and a threshold level of  $2/3V_{CC}$ . The control voltage input (*pin 5*) can be used to externally adjust the trigger and threshold levels to other values if necessary. When the normally **HIGH** trigger input momentarily goes below  $1/3V_{CC}$ , the output of comparator **B** switches from **LOW** to **HIGH** and set the **S-R** latch, causing the output (*pin 3*) to go **HIGH** and turning the discharge transistor  $Q_1$  off. The output will stay **HIGH** until the normally **LOW** threshold input goes above  $2/3V_{CC}$  and causes the output of comparator **A** to switch from **LOW** to **HIGH**. This resets the latch, causing the output to go back **LOW** and turning the discharge transistor on. The external reset input can be used to reset the latch independent of the threshold circuit. The trigger and threshold input (*pin 2 and 6*) are controlled by external components connected to produce either monostable or astable action.

### Monostable (One-Shot) Operation

An external resistor and capacitor connected as shown in Fig. (2) are used to set up the 555 timer as a non-retriggerable one-shot. The pulse width of the output is determined by the timer constant of  $R_1$  and  $C_1$  according to the following formula:

$$t_w = 1.1 R_1 C_1. \quad (1)$$

the control voltage input is not used and is connected to a decoupling capacitor  $C_2$  to prevent noise from affecting the trigger and threshold levels.

Before a trigger pulse is applied, the output is **LOW** and the discharge transistor  $Q_1$  is on, keeping  $C_1$  discharge as shown in Fig. (3a). When a negative-going trigger pulse is applied, the output goes **HIGH** and the discharge

transistor turns off, allowing capacitor  $C_1$  to begin charging through  $R_1$  as shown in Fig. (3b). When  $C_1$  charges to  $1/3V_{CC}$ , the output goes back **LOW** and  $Q_1$  turn on immediately, discharging  $C_1$  as shown in Fig. (3c). As you can see, the charging rate of  $C_1$  determines how long the output is **HIGH**.

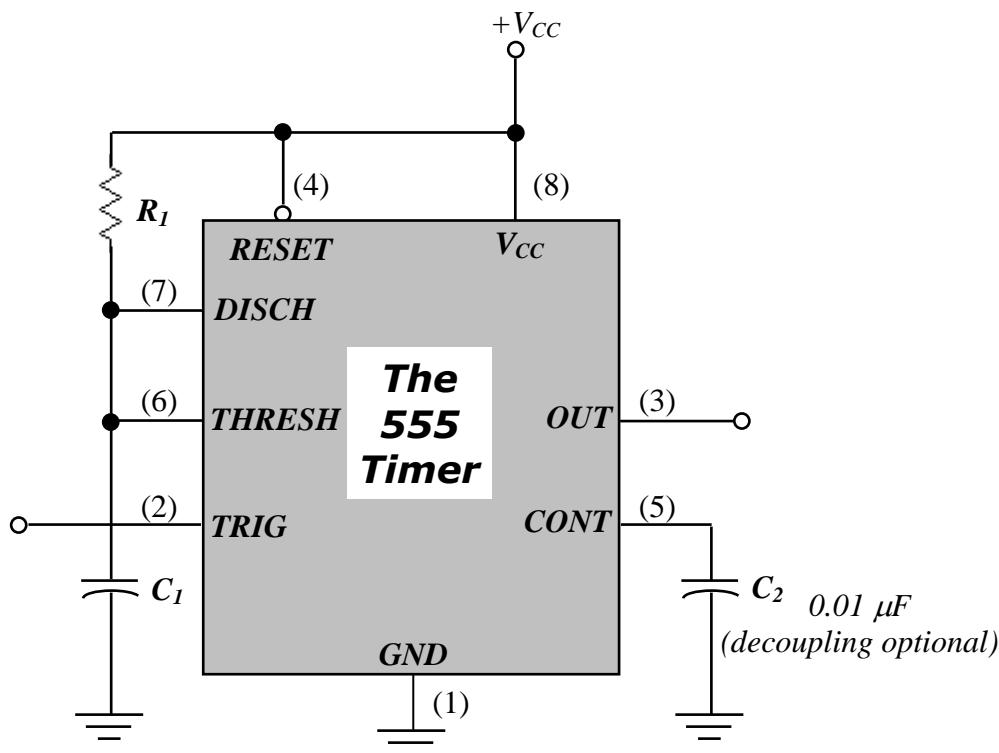


Fig. (2): The 555 timer connected as a one-shot.

### EXAMPLE.1

What is the output pulse width for a 555 monostable circuit with  $R_1=2.2\text{ k}\Omega$  and  $C_1=0.01\text{ }\mu\text{F}$ ?

#### Solution

From equation (1) the pulse width is

$$t_w=1.1 R_1.C_1=1.1*(2.2\text{ k}\Omega)*(0.01\text{ }\mu\text{F})=24.2\text{ }\mu\text{s}.$$

### Homework

For  $C_1=0.01\text{ }\mu\text{F}$ , determine the value of  $R_1$  for a pulse width of  $1\text{ ms}$ .

Fig. (3a): Prior for triggering.



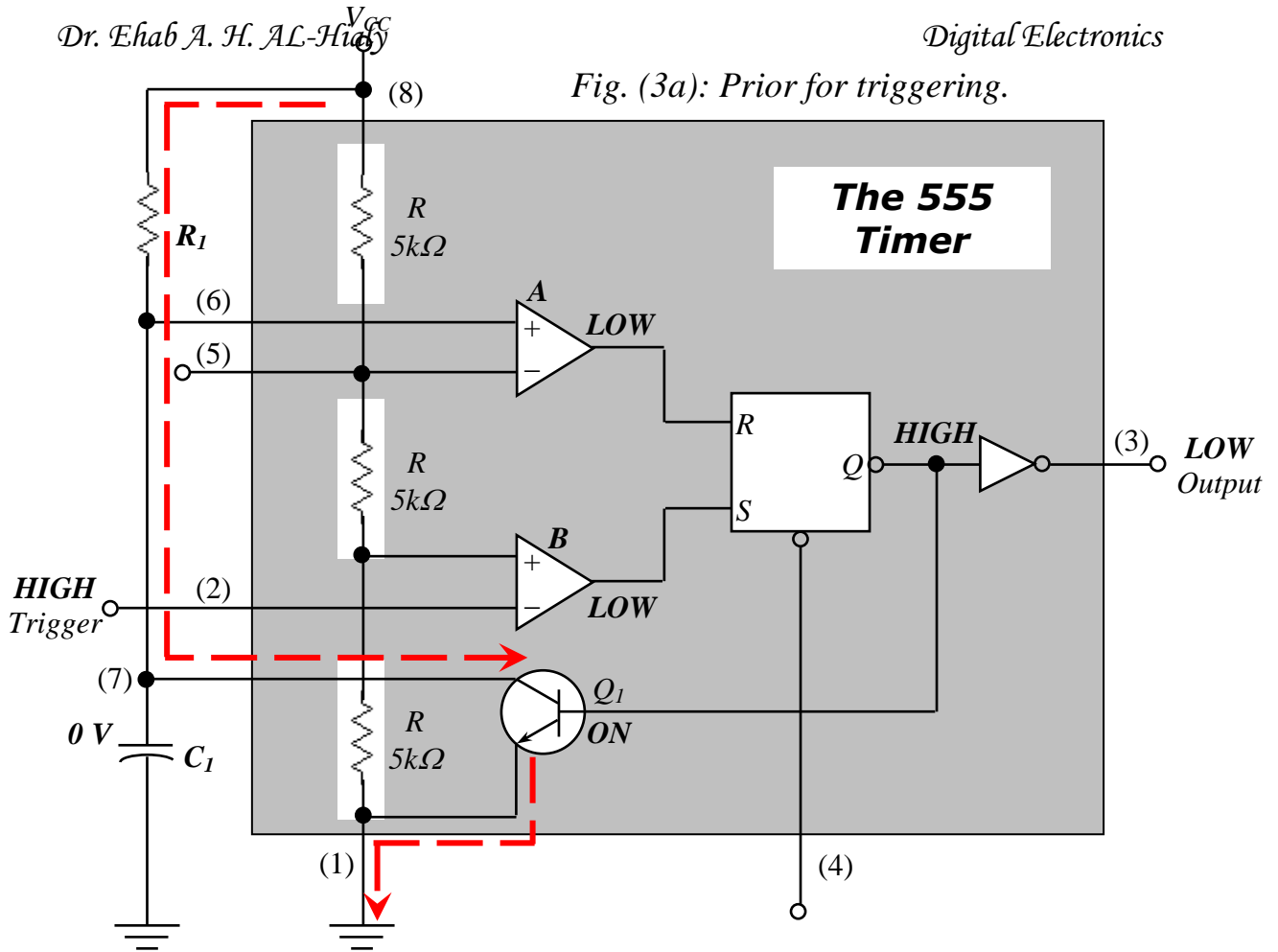


Fig. (3b): When triggered.

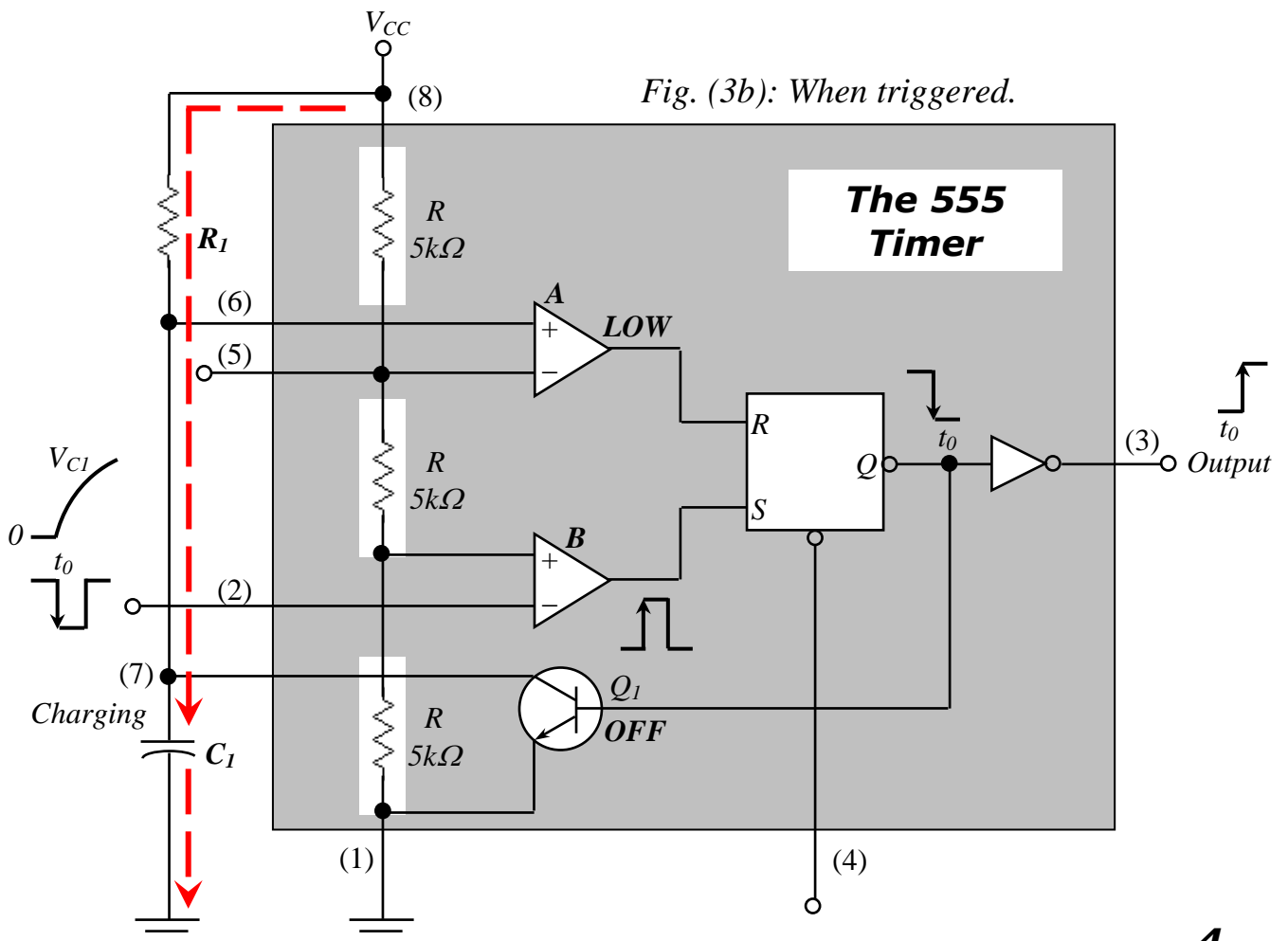

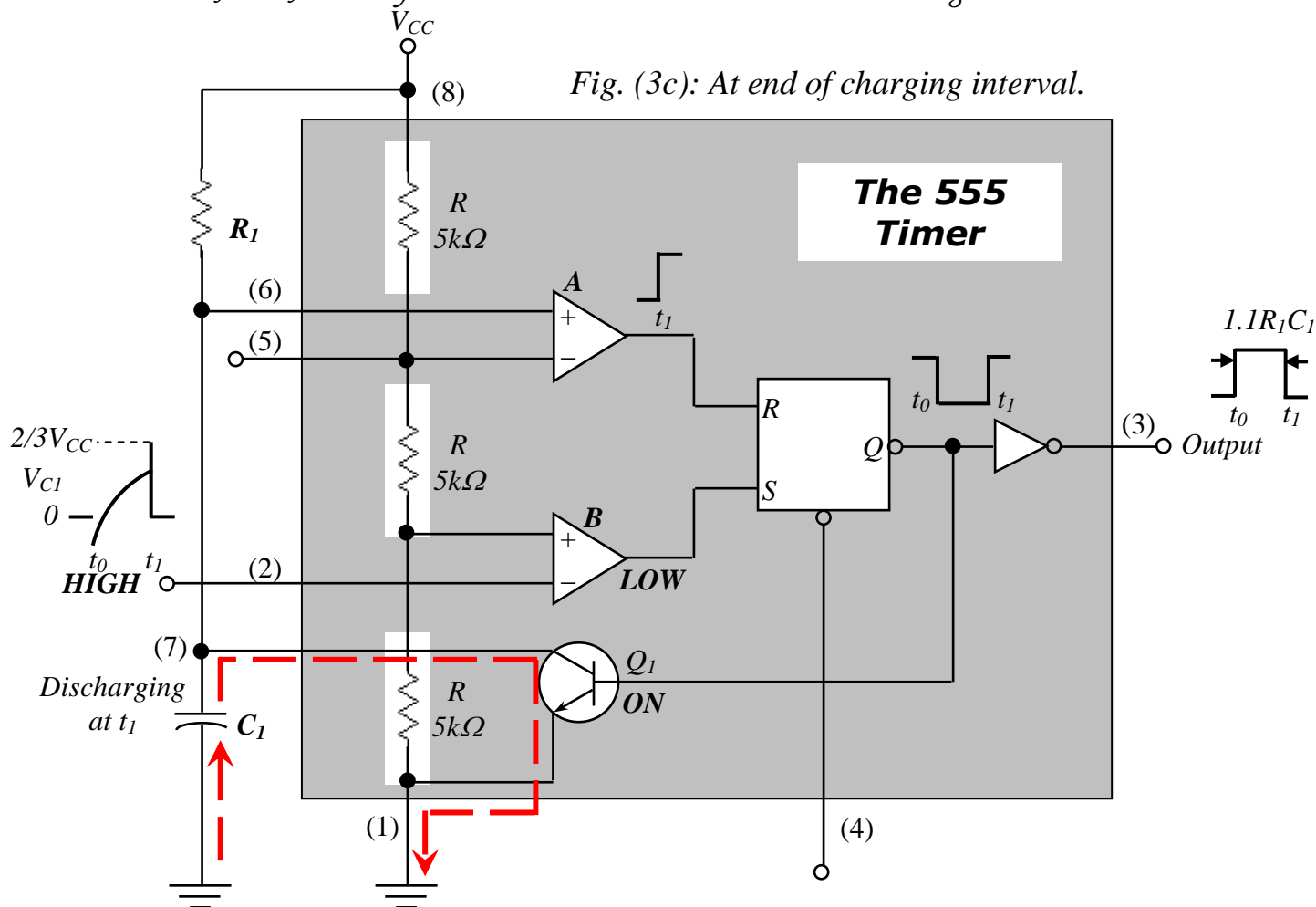

### Astable Operation

A 555 timer connected to operate as an *astable* multivibrator, which is a non-sinusoidal *oscillator*, is shown in Fig. (4). Notice that the threshold input (*THRESH*) is now connected to the trigger input (*TRIG*). The external components  $R_1$ ,  $R_2$ , and  $C_1$  from the timing network that sets the frequency of oscillation. The (0.01  $\mu\text{F}$ ) capacitor  $C_2$  connected to the control (*CONT*) input is strictly for decoupling and has no effect on the operation in some cases it can be left off.

Initially, when the power is turned on, the capacitor ( $C_1$ ) is uncharged and thus the trigger voltage (*pin 2*) is at (0 V). This causes the output of comparator **B** to be **HIGH** and the output of comparator **A** to be **LOW**, forcing the output of the latch, and thus the base of  $Q_1$ , **LOW** and keeping the transistor off. Now,  $C_1$

begins charging through  $R_1$  and  $R_2$  as indicated in Fig. (5). When the capacitor voltage reaches  $1/3 V_{CC}$ , comparator **B** switches to its **LOW** output state, and when the capacitor voltage reaches  $2/3 V_{CC}$ , comparator **A** switches to its **HIGH** output state. This resets the latch, causing the base of  $Q_1$  to go **HIGH** and turning on the transistor. This sequence creates a discharge path for the capacitor through  $R_2$  and the transistor, as indicated. The capacitor now begins to discharge, causing comparator **A** to go **LOW**. At the point where the capacitor discharges down to  $1/3 V_{CC}$ , comparator **B** switches **HIGH**; this sets latch, making the base of  $Q_1$  **LOW** and turning off the transistor. Another charging cycle begins, and the entire process repeats. The result is a rectangular wave output whose duty cycle depends on the values of  $R_1$  and  $R_2$ . The frequency of oscillation is given by the formula

$$f = \frac{1.44}{(R_1 + 2R_2)C_1} \quad (2)$$

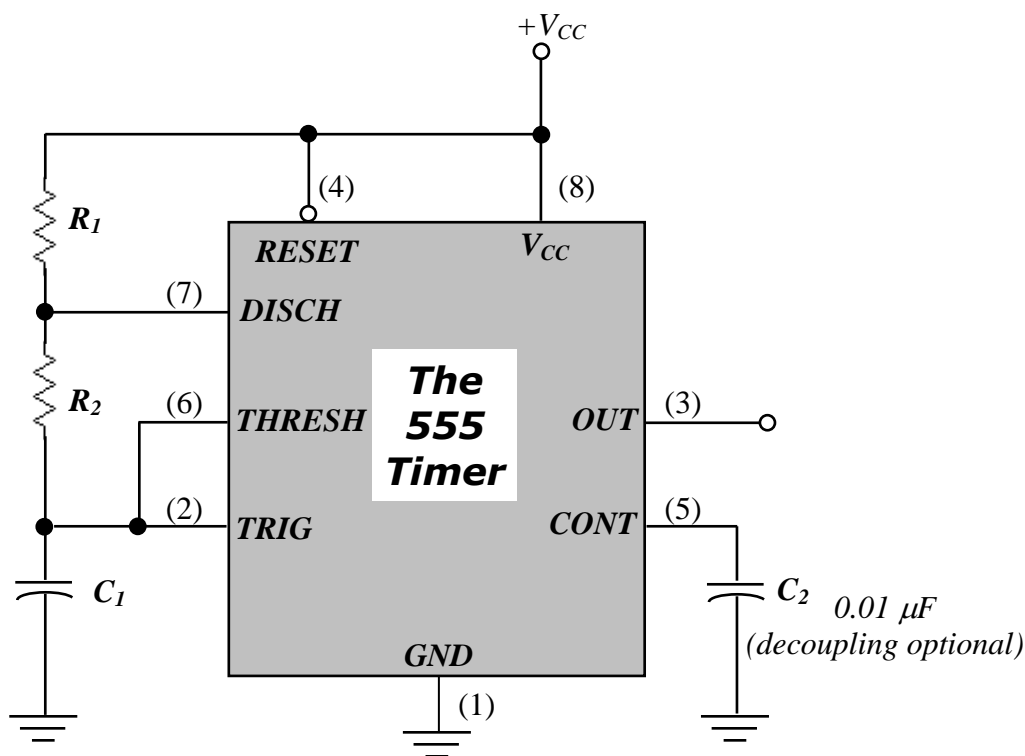


Fig. (4): The 555 timer connected as an astable multivibrator (oscillator).

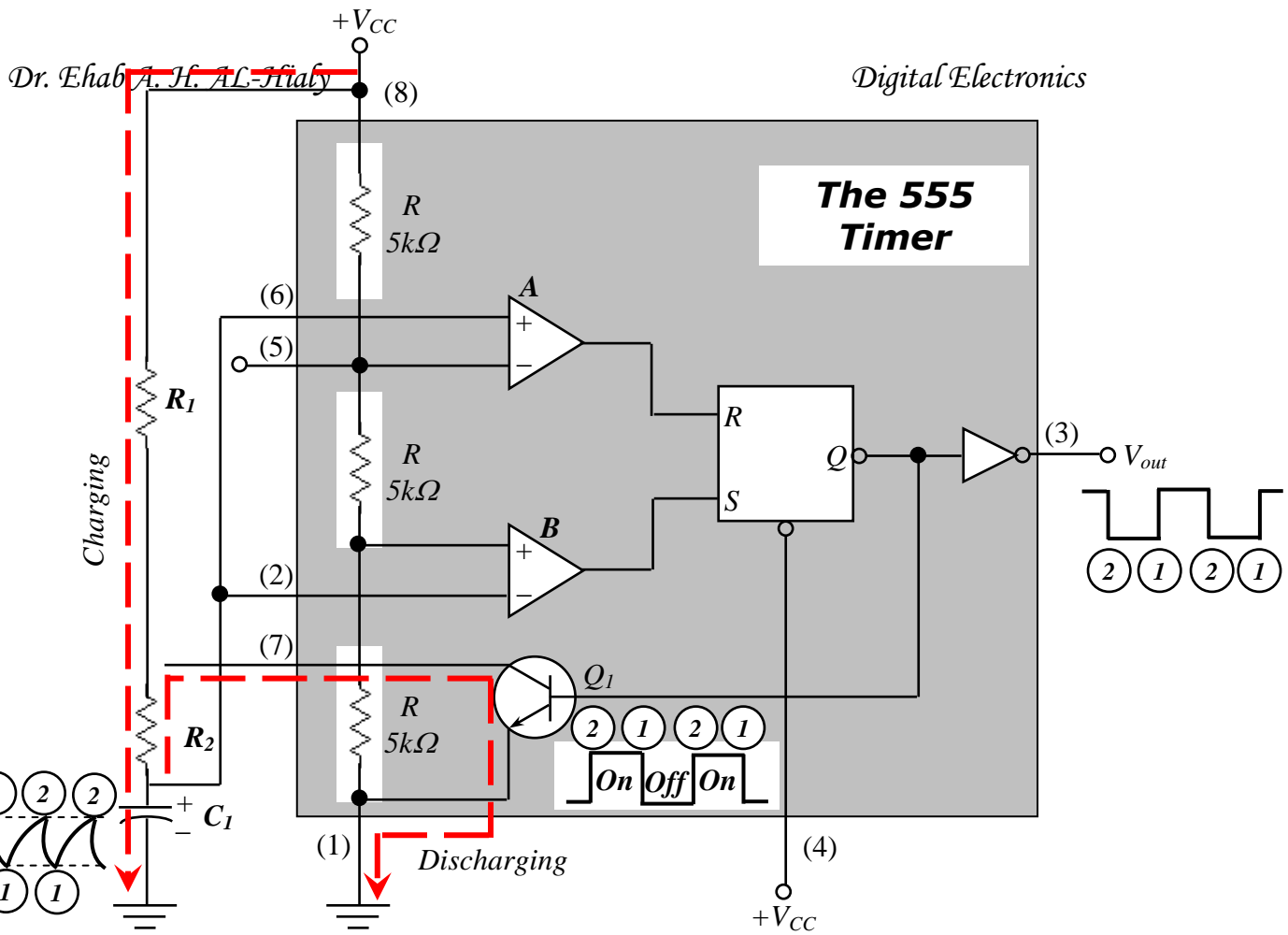


Fig. (5): Operation of 555 timer in the astable mode.

By selecting  $R_1$  and  $R_2$ , the duty cycle of the output can be adjusted. Since  $C_1$  charges through  $R_1+R_2$  and discharges only through  $R_2$ , duty cycles approaching a minimum of 50 percent can be achieved if  $R_2 \gg R_1$  so that the charging and discharging times are approximately equal.

An expression for the duty cycle is developed as follows. The time that the output is **HIGH** ( $t_H$ ) is how long it takes  $C_1$  to charge from  $1/3V_{CC}$  to  $2/3V_{CC}$ . It is expressed as

$$t_H = 0.7(R_1 + R_2)C_1. \quad (3)$$

The time that the output is **LOW** ( $t_L$ ) is how long it takes  $C_1$  to discharge from  $2/3V_{CC}$  to  $1/3V_{CC}$ . It is expressed as

$$t_L = 0.7R_2C_1. \quad (4)$$

The period,  $T$ , of the output waveform is the sum of  $t_H$  and  $t_L$ .

$$T = t_H + t_L = 0.7(R_1 + 2R_2)C_1. \quad (5)$$

This is the reciprocal of (f) in equation (2). Finally, the duty cycle is

$$Duty\ Cycle = \frac{t_H}{T} = \frac{t_H}{t_H + t_L}$$

$$Duty\ Cycle = \left( \frac{R_1 + R_2}{R_1 + 2R_2} \right) 100\% \tag{6}$$

To achieved duty cycles of less than 50 percent, the circuit in Fig. (4) can be modified so that  $C_1$  charges through only  $R_1$  and discharges through  $R_2$ . This is achieved with a diode  $D_1$  placed as shown in Fig. (6). The duty cycle can be made less than 50 percent by making  $R_1$  less than  $R_2$ . Under this expression for the duty cycle is

$$Duty\ Cycle = \left( \frac{R_1}{R_1 + R_2} \right) 100\%$$


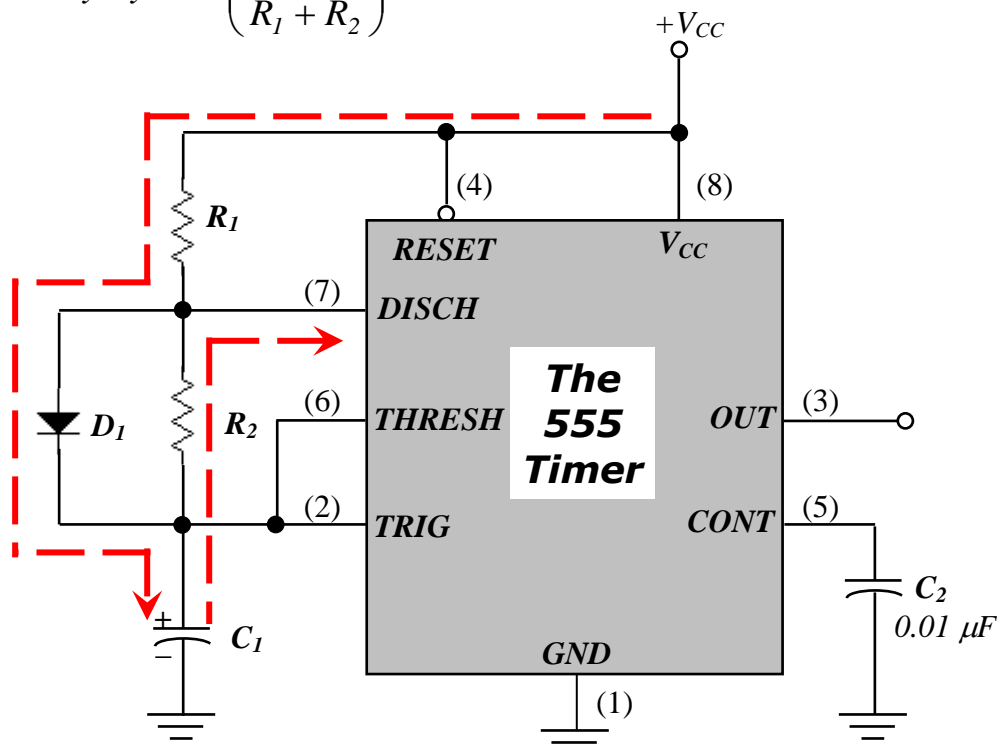


Fig. (6): The addition of diode  $D_1$  allows the duty cycle of the output to be adjusted to less than 50 percent by making  $R_1 < R_2$ .
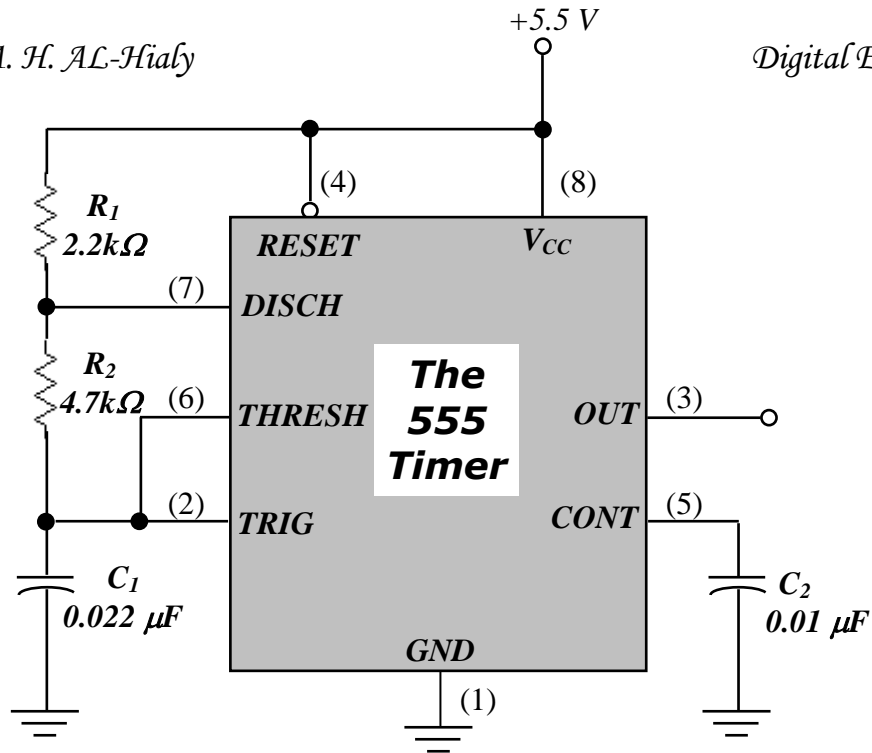
### EXAMPLE.2

A 555 timer configured to run in the astable mode (oscillator) is shown in figure below. Determine the frequency of the output and the duty cycle.





### Solution

Use Equations (2 and 6).

$$f = \frac{1.44}{(R_1 + 2R_2)C_1} = \frac{1.44}{(2.2k\Omega + 9.4k\Omega)0.022\mu F} = 5.64 \text{ kHz}$$

$$\text{Duty cycle} = \left( \frac{R_1 + R_2}{R_1 + 2R_2} \right) 100\% = \left( \frac{2.2k\Omega + 4.7k\Omega}{2.2k\Omega + 9.4k\Omega} \right) 100\% = 59.5\%$$

### Homework

Determine the duty cycle in figure above if a diode is connected across  $R_2$  as indicated in Fig. (6).