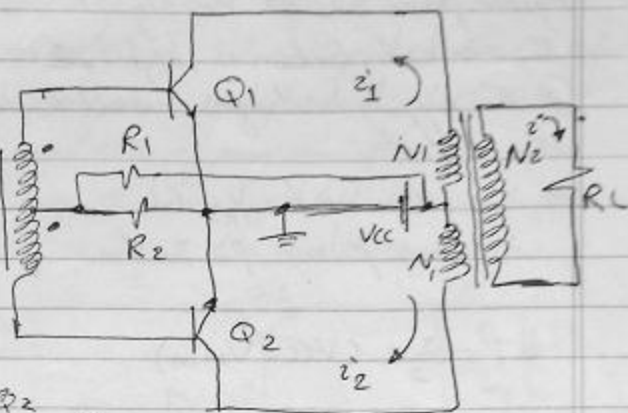


### 6.1.6 Push-Pull Amplifier :-

In this ckt the excitation is introduced through a center tapped transformer, so when the signal on trans.  $Q_1$  is positive, the signal on  $Q_2$  is negative by an equal amount.



we have  $e_{b1} = I_{bm} \cos \omega t$

$$\therefore i_1 = I_C + B_0 + B_1 \cos \omega t + B_2 \cos 3\omega t + \dots$$

$$\therefore e_{b2} = -e_{b1} = I_{bm} \cos(\omega t + \pi)$$


$$\therefore i_2 = I_C + B_0 - B_1 \cos \omega t - B_2 \cos 3\omega t - \dots$$

$$e = K(i_1 - i_2) = 2K(B_1 \cos \omega t + B_3 \cos 3\omega t + \dots)$$

This expression shows that a push-pull circuit will balance out all even harmonics in the op and will leave the third-harmonic term as the principle source of distortion.
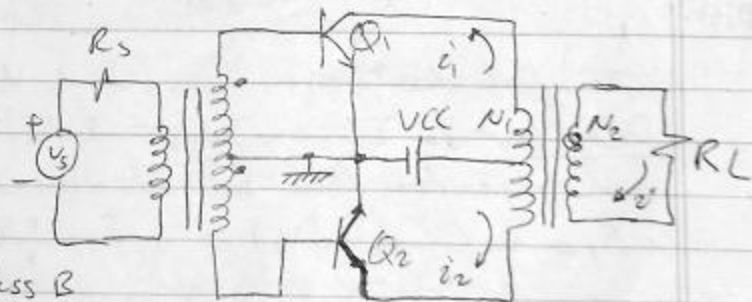
### 6.2 Class B Amplifier

The silicon Trans. is at cut off of the base is shorted to the emitter.



The advantages of class B over compared with class A operation are the following:

- ① Greater power op. ② higher efficiency, ③ There is negligible power loss at no signal. The disadvantages are ① the harmonic distortion is higher, ② self bias cannot be used, ③ The supply voltages must have good regulation.

we have  $RL' = Y_R RL$


The o/p power  $P = \frac{I_m V_m}{2}$

$\therefore P = \frac{I_m}{2} (V_{CC} - V_{min})$

$P_i$  = dc input power from the supply

$P_i = 2 I_{dc} V_{CC}$

$P_i = \frac{2 I_m V_{CC}}{\pi}$

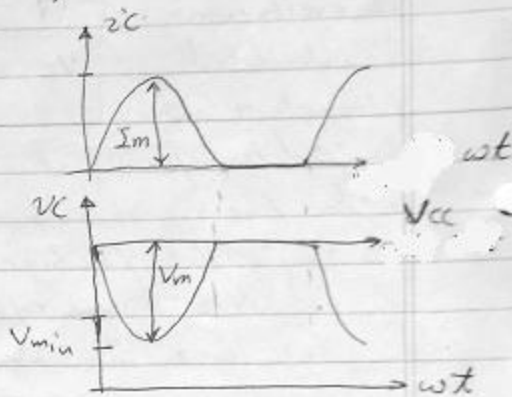

without Distortion.  $\eta = \frac{P}{P_i} \times 100\% = \frac{\pi}{4} \frac{V_m}{V_{CC}} = \frac{\pi}{4} (1 - \frac{V_{min}}{V_{CC}}) \times 100\%$

The dissipation Power ( $P_c$ ) is given by  $P_c = P_i - P$

$P_c = 2 \frac{I_m V_{CC}}{\pi} - \frac{I_m V_m}{2}$  and since  $I_m = \frac{V_m}{RL'}$

without Dist.  $\therefore P_c = 2 \frac{V_m V_{CC}}{\pi RL'} - \frac{V_m^2}{2 RL'}$

The peak dissipation  $P_{cmax} = 2 V_{CC}^2 / \pi^2 RL'$  when  $V_m = \frac{2 V_{CC}}{\pi}$

Distortion:  $I_C = 0$ ,  $I_{max} = -I_{min}$ ,  $I_{V_2} = I - \frac{1}{2}$  for 5th order distortion then  $B_0 = B_2 = B_4 = 0$ , and

$B_1 = \frac{2}{3} (I_{max} + I_{V_2})$ ,  $B_3 = \frac{1}{3} (I_{max} - 2 I_{V_2})$

with Distortion  $\therefore P = \frac{(1 + D_3^2) B_1^2 RL'}{2}$

$\eta = \frac{P}{P_i} \times 100\% = \frac{(1 + D_3^2) B_1^2 RL' / 2}{2 \frac{I_{max} V_{CC}}{\pi}} \times 100\%$

**Ex**

A Transformer-Coupled Audio power amplifier operating Class A<sub>2</sub> is designed to deliver a maximum of 5 watt to a 4Ω load.  $V_{CC} = 20V$ .  $V_{min} = 0$

(a) what is the turn ratio of the transformer  $n$ ?

(b) what is the peak collector current  $I_m$ ?

(c) determine  $I_C$ ,  $V_{CE}$ ?

(d) determine  $\eta$ , without Distortion.

Solution:

$$(a) P = \frac{1}{2} \frac{V_m^2}{R_L'}$$

$$V_C = V_{CC} = 20V = V_m$$

$$\therefore P = \frac{1}{2} \times \frac{400}{R_L'} = 5$$

$$\therefore R_L' = \frac{400}{10} = 40 = \frac{R_L}{n^2} \Rightarrow n = \sqrt{R_L/R_L'}$$



$$(b) P = \frac{1}{2} I_m^2 R_L' \Rightarrow I_m^2 = 2P/R_L' = 10/40 = 1/4$$

$$\therefore I_m = 0.5 A$$

$$(c) I_C = I_m = 0.5 A$$

$$V_{CE} = V_C = 20V$$

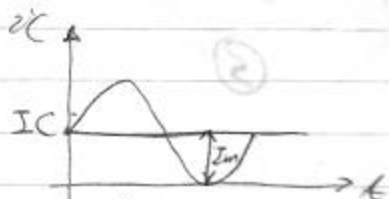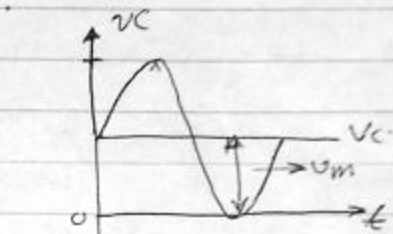
$$(d) \eta = \frac{5}{20 \times 0.5} = 0.5 = 50\% = \frac{P_o}{P_i} \times 100\% = \frac{5}{V_{CC} I_C} \times 100\%$$



waveform

**Ex** The power Trans. whose  $i_C$  and  $V_C$  are given and used in the class B push-pull ckt. with  $V_{CC} = 20V$ ,

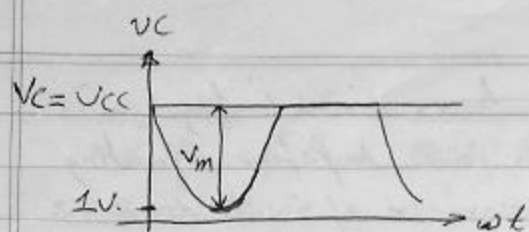if the Base Current is sinusoidal, with the peak value of 20mA,  $R_L' = 15\Omega$ . (a) The third-harmonic distortion, (b) the power o/p. with Distortion, (c) the  $\eta$ , without Distortion.



$$I_{max} = 1.26 \text{ A}, I_{V_2} = 0.75 \text{ A}.$$

Solution is (a)

$$B_3 = \frac{1}{3} (I_{max} - 2I_{V_2}) = \frac{1}{3} (1.26 - 1.5) = -80 \text{ mA}.$$

$$B_1 = \frac{2}{3} (I_{max} + I_{V_2}) = \frac{2}{3} (1.26 + 0.75) = 1.34 \text{ A}.$$

$$D_3 = \frac{|B_3|}{|B_1|} = \frac{80}{1340} = 5.97\%.$$

$$(b) P = (1 + D_3^2) \frac{B_1^2 R_L'}{2} = (1 + 0.00356) (1.34)^2 \times \frac{15}{2}$$

$$\therefore P = 13.51 \text{ watt}.$$

(c)

$$\eta = \frac{\pi}{4} \left( 1 - \frac{V_{min}}{V_{cc}} \right) \times 100\% = \frac{\pi}{4} \left( 1 - \frac{1}{20} \right) \times 100\% = 74.61\%.$$

$P_{without}$

$$P = \frac{I_m}{2} (V_{cc} - V_{min})$$

$$= \frac{1.26}{2} (20 - 1) = 11.97 \text{ watt}.$$

$$\eta_{with} = \frac{P_{with}}{P_i} = \frac{13.51}{(2 \times 15 \times 4/\pi)} = 84.17\%.$$