

## TRANSMISSION LINE

### 1. Telegraph Equations

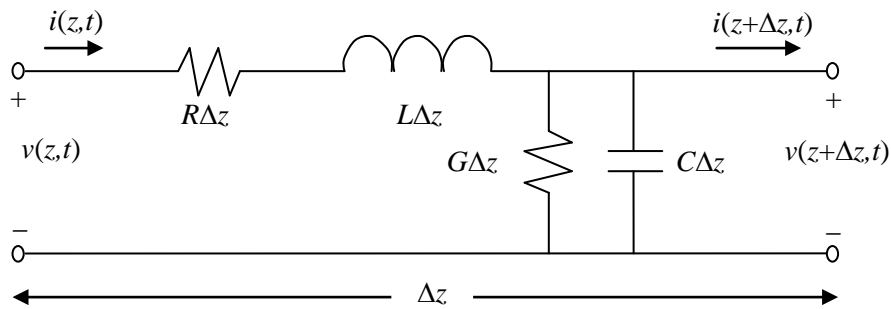


Fig.(1.1)

From the circuit of Fig.(1.1), *Kirchhoff's* voltage law can be applied to give

$$v(z, t) - R\Delta z i(z, t) - L\Delta z \frac{\partial i(z, t)}{\partial t} - v(z + \Delta z, t) = 0 \quad (1a)$$

and *Kirchhoff's* current law leads to

$$i(z, t) - G\Delta z v(z + \Delta z, t) - C\Delta z \frac{\partial v(z + \Delta z, t)}{\partial t} - i(z + \Delta z, t) = 0 \quad (1b)$$

Dividing Eq.(1a) and (1b) by  $\Delta z$  and taking the limit as  $\Delta z \rightarrow 0$  gives the following differential equations:

$$\frac{\partial v(z, t)}{\partial z} = -R i(z, t) - L \frac{\partial i(z, t)}{\partial t} \quad (2a)$$

$$\frac{\partial i(z, t)}{\partial z} = -G v(z, t) - C \frac{\partial v(z, t)}{\partial t} \quad (2b)$$

For the sinusoidal steady-state condition, with cosine-based phasors, Eq.(2) simplify to

$$\frac{dV(z)}{dz} = -(R + j\omega L)I(z) = -Z I(z) \quad (3a)$$

$$\frac{dI(z)}{dz} = -(G + j\omega C)V(z) = -Y V(z) \quad (3b)$$

Where,  $Z = R + j\omega L$ , impedance of the line per-unit length  $\Omega/m$

$Y = G + j\omega C$ , admittance of the line per-unit length  $S/m$

From Eq.(3)

$$\frac{d^2V(z)}{dz^2} = -Z \frac{dI(z)}{dz} = Z Y V(z) \quad (4a)$$

$$\frac{d^2I(z)}{dz^2} = -Y \frac{dV(z)}{dz} = Z Y I(z) \quad (4b)$$

Let  $V(z) = e^{\gamma z}$ , and solving for the second order homogenous differential Equation (4a) gives

$$V(z) = \underbrace{\vec{V}_0 e^{-\gamma z}}_{\text{incident voltage}} + \underbrace{\vec{V}_0 e^{\gamma z}}_{\text{reflected current}} = \vec{V}(z) + \vec{V}(z) \quad (5)$$

Where  $\gamma$  (propagation constant)  $= \sqrt{ZY} = \sqrt{(R + j\omega L)(G + j\omega C)} = \alpha + j\beta$ ,  $\vec{V}_0$  and  $\vec{V}_0$  are the integration constants. Substituting the derivative of  $V(z)$  from Eq.(5) in Eq.(3a) the current equation is found as

$$I(z) = \frac{\gamma}{Z} [\vec{V}_0 e^{-\gamma z} - \vec{V}_0 e^{\gamma z}] = \vec{I}(z) + \vec{I}(z) \quad (6)$$

Defining the *characteristic impedance*

$$Z_0 = \frac{\vec{V}(z)}{\vec{I}(z)} = \frac{\vec{V}_0 e^{-\gamma z}}{\frac{\gamma}{Z} \vec{V}_0 e^{-\gamma z}} = \frac{Z}{\gamma} = \frac{Z}{\sqrt{ZY}} = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{(R + j\omega L)}{(G + j\omega C)}} \quad (7)$$

Where  $\alpha$  is the *attenuation constant*, and  $\beta$  is the *phase constant*.

For lossless transmission line (T.L),  $R=G=0$ , then  $\alpha = 0$ . Substitute Eq.(7) in (6) gives

$$I(z) = \frac{1}{Z_0} [\vec{V}_0 e^{-\gamma z} - \vec{V}_0 e^{\gamma z}] \quad (8)$$

## 2. Phase Velocity and Wavelength on the T.L

The time varying signal on the line is

$$\begin{aligned} v(z, t) &= V(z) e^{j\omega t} \\ &= [\vec{V}_0 e^{-\gamma z} + \vec{V}_0 e^{\gamma z}] e^{j\omega t} \end{aligned} \quad (9)$$

Substituting  $\gamma = \alpha + j\beta$  in Eq.(9) yield

$$v(z, t) = \underbrace{\vec{V}_0 e^{-\alpha z} \cdot e^{j(\omega t - \beta z)}}_{\text{incident}} + \underbrace{\vec{V}_0 e^{\alpha z} e^{j(\omega t + \beta z)}}_{\text{reflected}} \quad (10)$$

Let the phase  $\phi(t) = \omega t - \beta z$ , then  $\frac{d\phi(t)}{dt} = \omega - \beta \frac{dz}{dt}$ . Extreme value when  $\frac{d\phi(t)}{dt} = 0$ ,

$$0 = \omega - \beta \frac{dz}{dt} \Rightarrow \frac{dz}{dt} = \frac{\omega}{\beta}$$

Define the *phase velocity*


$$v_p = \frac{dz}{dt} = \frac{\omega}{\beta} = f \cdot \lambda_g \quad (11)$$

From Eq.(11),  $\frac{\omega}{\beta} = \frac{2\pi f}{\beta} = f \cdot \lambda_g \Rightarrow \beta = \frac{2\pi}{\lambda_g}$
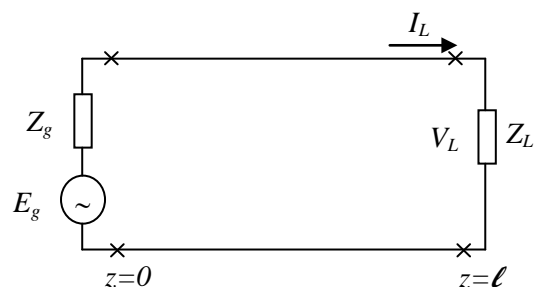
## 3. Determination of Integration Constants ( $\vec{V}_0$ and $\vec{V}_0$ )

In order to determine these two constants, we need to know the current and the voltage at any point on the T.L. Usually, these constants are determined either from the current and voltage at load side or at the generator side.

Let us assume that the voltage and the current at the load side ( $z=\ell$ )  $V_L$  and  $I_L$  are known, then



From Eq.(5) and (8)

$$V_L = \vec{V}_o e^{-\gamma\ell} + \tilde{V}_o e^{\gamma\ell} \quad (12)$$

$$I_L Z_o = \vec{V}_o e^{-\gamma\ell} - \tilde{V}_o e^{\gamma\ell} \quad (13)$$

Adding Eq.(12) to (13), we get

$$V_L + Z_o I_L = 2\vec{V}_o e^{-\gamma\ell} \quad \Rightarrow \quad \vec{V}_o = \left[ \frac{V_L + Z_o I_L}{2} \right] e^{\gamma\ell}$$

Subtracting Eq.(13) from (12), then

$$\tilde{V}_o = \left[ \frac{V_L - Z_o I_L}{2} \right] e^{-\gamma\ell}$$

Now substituting  $\vec{V}_o$  and  $\tilde{V}_o$  in Eq.(5) yields

$$V(z) = \left[ \frac{V_L + Z_o I_L}{2} \right] e^{\gamma\ell} e^{-\gamma z} + \left[ \frac{V_L - Z_o I_L}{2} \right] e^{-\gamma\ell} e^{\gamma z}$$

$$V(z) = V_L \frac{e^{\gamma(\ell-z)} + e^{-\gamma(\ell-z)}}{2} + Z_o I_L \frac{e^{\gamma(\ell-z)} - e^{-\gamma(\ell-z)}}{2}$$

$$V(z) = V_L \cosh[\gamma(\ell - z)] + Z_o I_L \sinh[\gamma(\ell - z)] \quad (14)$$

Similarly, one can get for  $I(z)$

$$I(z) = I_L \cosh[\gamma(\ell - z)] + \frac{V_L}{Z_o} \sinh[\gamma(\ell - z)] \quad (15)$$


**H.W:** Try to find  $\vec{V}_o$  and  $\tilde{V}_o$  in terms of generator side.

#### 4. Impedance Along the T.L

The input impedance at any point along the T.L is given by;

$$Z(z) = \frac{V(z)}{I(z)} = Z_o \frac{\vec{V}_o e^{-\gamma z} + \tilde{V}_o e^{\gamma z}}{\vec{V}_o e^{-\gamma z} - \tilde{V}_o e^{\gamma z}}$$

or

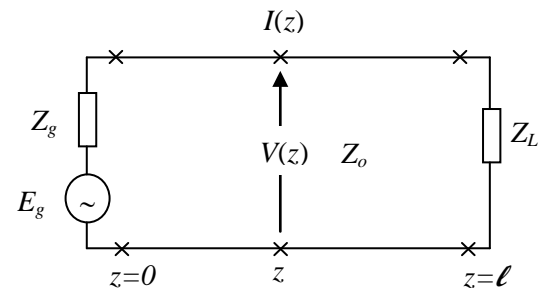

$$Z(z) = \frac{V_L \cosh[\gamma(\ell - z)] + Z_o I_L \sinh[\gamma(\ell - z)]}{I_L \cosh[\gamma(\ell - z)] + \frac{V_L}{Z_o} \sinh[\gamma(\ell - z)]}$$

$$Z(z) = \frac{V_L + Z_o I_L \tanh[\gamma(\ell - z)]}{I_L + \frac{V_L}{Z_o} \tanh[\gamma(\ell - z)]}$$

dividing by  $I_L$ , we get

$$Z(z) = \frac{\frac{V_L}{I_L} + Z_o \tanh[\gamma(\ell - z)]}{1 + \frac{V_L}{I_L Z_o} \tanh[\gamma(\ell - z)]}$$

Since  $\frac{V_L}{I_L} = Z_L$ , then

$$Z(z) = \frac{Z_L + Z_o \tanh[\gamma(\ell - z)]}{1 + \frac{Z_L}{Z_o} \tanh[\gamma(\ell - z)]} = Z_o \frac{Z_L + Z_o \tanh[\gamma(\ell - z)]}{Z_o + Z_L \tanh[\gamma(\ell - z)]}$$

or

$$Z(z) = Z_o \frac{Z_L \cosh[\gamma(\ell - z)] + Z_o \sinh[\gamma(\ell - z)]}{Z_o \cosh[\gamma(\ell - z)] + Z_L \sinh[\gamma(\ell - z)]} \quad (16)$$

The impedance at  $z = 0$  (at the generator) is

$$Z(0) = Z_{in} = Z_o \frac{Z_L \cosh \gamma \ell + Z_o \sinh \gamma \ell}{Z_o \cosh \gamma \ell + Z_L \sinh \gamma \ell} \quad (17)$$

For lossless T.L,  $\alpha = 0 \Rightarrow \gamma = j\beta$ ,

and  $\cosh(j\beta\ell) = \cos\beta\ell$ , also  $\sinh(j\beta\ell) = j \sin\beta\ell$ , therefore;

$$Z_{in} = Z_o \frac{Z_L \cos\beta\ell + jZ_o \sin\beta\ell}{Z_o \cos\beta\ell + jZ_L \sin\beta\ell} = Z_o \frac{Z_L + jZ_o \tan\beta\ell}{Z_o + jZ_L \tan\beta\ell} \quad (18)$$

### 5. Reflection Coefficient ( $\Gamma$ )

The amplitude of the reflected voltage wave normalized to the amplitude of the incident voltage wave is defined as the voltage reflection coefficient,  $\Gamma$ :

$$\begin{aligned} \Gamma_V &= \frac{\tilde{V}(z)}{\vec{V}(z)} = \frac{\tilde{V}_o e^{\gamma z}}{\vec{V}_o e^{-\gamma z}} \\ &= \frac{\left[ \frac{V_L - Z_o I_L}{2} \right] e^{-\gamma \ell} e^{\gamma z}}{\left[ \frac{V_L + Z_o I_L}{2} \right] e^{\gamma \ell} e^{-\gamma z}} = \left[ \frac{V_L - Z_o I_L}{V_L + Z_o I_L} \right] e^{-2\gamma(\ell - z)} \end{aligned}$$

Let  $y = \ell - z$ , then

$$\Gamma_V = \left[ \frac{V_L - Z_o I_L}{V_L + Z_o I_L} \right] e^{-2\gamma y} = \left[ \frac{Z_L - Z_o}{Z_L + Z_o} \right] e^{-2\gamma y}$$

At load ( $y = 0$ ),  $\Gamma_{V0} = \left[ \frac{Z_L - Z_o}{Z_L + Z_o} \right]$ , therefore

$$\Gamma_V = \Gamma_{V0} e^{-2\gamma y} \quad (19)$$

If  $Z_L = Z_o$ , results that  $\Gamma_{V0} = 0$ , i.e., the load impedance is matched to the characteristic impedance.

For lossless T.L.,  $\Gamma_V = \Gamma_{V0} e^{-2j\beta y}$ , the reflection coefficient has constant magnitude along the line but with different phase.

Similarly the current reflection coefficient

$$\Gamma_I = \frac{\tilde{I}(z)}{\vec{I}(z)} = \frac{-\frac{1}{Z_o} \tilde{V}_o e^{\gamma z}}{\frac{1}{Z_o} \vec{V}_o e^{-\gamma z}} = -\frac{\tilde{V}_o}{\vec{V}_o} e^{2\gamma z}$$

After substituting  $\tilde{V}_o$  and  $\vec{V}_o$ , one can get

$$\Gamma_I = -\Gamma_{I0} e^{-2\gamma y} \quad (20)$$

Therefore,  $\Gamma_I = -\Gamma_V$